

I. Before you come to lab

- Read this write up and the background material.

II. Learning Objectives

In this lab, you'll gain familiarity with circuits by solving two "puzzles" involving measuring some unknown quantities. The key to solving these puzzles will be a good understanding of circuits, both on a theoretical and a practical basis. You will also investigate the behavior of an RC circuit as a function of time.

III. Materials

Differential voltage probe

The differential voltage probe is basically just a voltmeter that interfaces with Logger Pro. Like the multimeter you used in Lab1, it measures the potential at the red probe minus the potential at the black probe.

Selection of alligator clip leads

Large 6 Volt Battery pack

2 Light Bulbs

Selection of resistors


The resistance of a resistor is indicated by the set of four colored stripes on the resistor. For an overview on how to read the value of the resistance from these colored stripes, refer to the supplemental.

1 "mystery" resistor

RC circuit board

This is a board wired with the circuit at μF , and the battery is a standard 1.5-volt

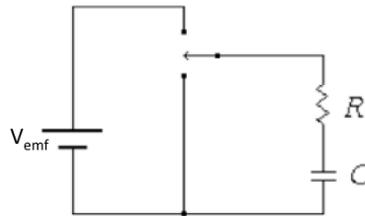When the switch is in the up position, the charge the capacitor. When the switch is in discharges through the resistor. When the no current flows and any charge which capacitor remains there.



right, where: $R = 30 \text{ k}\Omega$, $C = 1$ AA cell battery.

battery is included in the circuit to the down position, the capacitor happens to already be on the

V. Procedure

Who are you? (Picture, names, and emails please)

A:

Part 1: How bright?

Connect the battery to one light bulb by creating a closed circuit between them. **What happens?**

A:

If you were to attach a second light bulb (don't actually do it yet), so it is in series with the first, **how many times brighter or dimmer do you think the two bulbs would now shine, compared to the first one? Why?** (Consider the lights as identical resistors).

A:

Now attach a second light bulb, so it is in series with the first. **What do you notice about the brightness of the two bulbs versus the original brightness of one bulb? Does this match your prediction?**

A:

If you were to put the two bulbs in parallel with the battery (don't actually do it yet), **how many times brighter or dimmer do you think the two bulbs would now shine, compared to the single bulb in series? Why?**

A:

Now detach the second bulb and reattach it so it is in parallel with the first. **What do you notice about the brightness of the two bulbs versus the original brightness of one bulb? Does this match your prediction?**

A:

Which of the three setups (one bulb, two in series, two in parallel) draws the most power from the battery?

A:

Do you think the outlets in houses are wired in series or parallel? Why?

A:

Part 2: Mystery resistor

In this part of lab, you will attempt to determine the value of an unknown resistance by designing one or more circuits involving the mystery resistor and making appropriate measurements. Be forewarned: it's not trivial.

The tools you will be able to use to measure the mystery resistor are:

A battery pack

A selection of resistors of different (known) values

LabPro interface with differential voltage probe and the Logger Pro software. (Note that the only measurements you can make are *voltage* measurements. You cannot make direct measurements of current or resistance!)

Play around with the components at your disposal and see what you can measure. At some point, however, work with your lab partners to devise a systematic plan to determine the mystery resistance. Then put your plan into action!

Describe your procedure here; be specific! Include snapshots of circuit diagrams if you need to. Feel free to add as many steps as you need.

A:

Record your measurements and calculations here.

A:

What is the mystery resistance R?

R =

Part 3: Charging and discharging of a capacitor

In this part of the lab you will use an RC circuit board to explore the processes of charging and discharging a capacitor. You will also find the time constant for this circuit. Make sure you familiarize yourself with the RC circuit as described in the "Materials" and "Procedures" parts of the write up before taking data. You will use Logger Pro, but before collecting data, go into "Data Collection" and increase "samples/second" to 30 or more.

Charging RC

Start with the capacitor fully discharged. Connect the differential voltage probe in order to measure the voltage **across the capacitor** and click on Collect. While you are collecting data, throw the switch into the charging position.

What are the "initial" and "final" values of the capacitor voltage?

A:

What functional form does the plot look like (for the part where it's charging, not before charging)?

A:

How long after you throw the switch does it take for the capacitor voltage to go 63% of the way from its initial to final values?

A:

Is this consistent with the stated component values for R (30 k Ω) and C (1 microfarad)? Explain.

A:

Paste the relevant part of your graph here, including a curve fit:

A:

Discharging RC

Start with the capacitor fully charged. To minimize any error caused by slow discharge (see supplemental and Warm-up for explanation), keep the switch in the charging position until you are ready to throw it into the discharging position. It's okay if the voltage goes down a little bit before the discharging begins; it is as if the initial charge on the capacitor were somewhat lower. While you are collecting data, throw the switch into the discharging position.

How long does it take for the capacitor voltage to become 1/e of its initial value?

A:

Is the time constant the same as it was for charging? Explain.

A:

Paste the relevant part of your graph here, including a curve fit:

A:

VI. Conclusion

What is the most important thing you learned in lab today?

A:

Do you have any other comments to help us improve the lab experience for you?

A: